

## SEMESTER END EXAMINATIONS - MAY 2023

**Program : B.E. - Common to all Programs**  
**Course Name : Introduction to Electrical Engineering**  
**Course Code : ESC132**

**Semester : I**  
**Max. Marks : 100**  
**Duration : 3 Hrs**

### Instructions to the Candidates:

- Answer one full question from each unit.

### UNIT - I

- With neat diagram, briefly explain the following methods of electric power generation i) Nuclear ii) Solar. CO1 (10)
  - What is electrical load? Explain the loads based on type of utility. CO1 (10)
- Draw single line representation of power system. Briefly explain its components. CO1 (10)
  - With neat diagram, briefly explain the hydel electric power generation. CO1 (06)
  - Define electrical grid. List the types of electrical grid. CO1 (04)

### UNIT - II

- Find the current through the  $6\Omega$  resistor connected across AB in Fig.3(a) using Thevenin's theorem. CO2 (08)

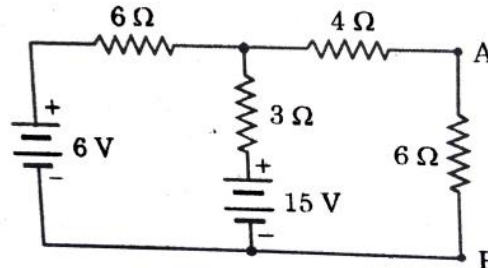


Fig. 3(a)

- Two batteries of A & B are connected in parallel to supply a load resistance of  $6\Omega$ . Draw the circuit arrangement. Calculate the current supplied by each battery and the load if the emfs. of A & B are 40 & 44 respectively. The internal resistance of A being  $2\Omega$  and that of B is  $4\Omega$ . CO2 (08)
  - State KVL and KCL. CO2 (04)
- State and explain: CO2 (10)  
(i) maximum power transfer theorem (ii) super position theorem.
  - Find the current through the resistor  $R=20\Omega$  for the circuit shown in Fig. 4(b) using superposition theorem. CO2 (10)

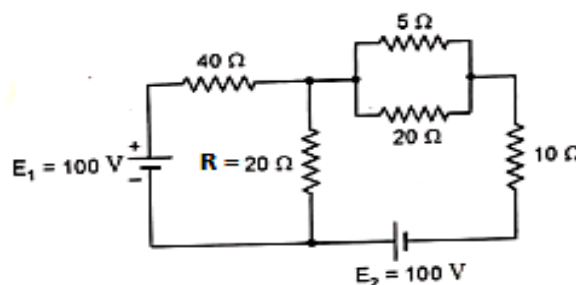


Fig.4(b)

## UNIT - III

5. a) With a neat diagram, derive an expression for the relationship between voltage and current in a series RLC circuit for  $X_L > X_C$  and obtain the expression for power. Draw the waveforms of voltage, current and power. CO2 (08)
- b) A resistance of  $24\Omega$ , an inductance of  $0.16H$  and a capacitance of  $150\mu F$  are connected in series across  $240V$ ,  $50Hz$  supply. Determine (i) impedance (ii) current (iii) voltage across R, L and C (iv) power in Watts and VA (v) power factor and angle of lag. CO2 (08)
- c) Define peak factor and form factor of sinusoidal quantities. CO2 (04)
6. a) Two impedances  $20\angle 45^\circ\Omega$  and  $30\angle 30^\circ\Omega$  are connected in series across a certain supply and the resulting current is found to be  $10A$ . If the supply voltage remains unchanged, calculate the supply current when the impedances are connected in parallel. CO2 (08)
- b) Define active, reactive and apparent power in an AC circuit indicating their units. An inductive circuit draws  $10A$  and  $1kW$  from a  $200V$ ,  $50Hz$  supply. Determine the (i) the impedance of the circuit in rectangular form ( $a+jb$ ) (ii) impedance in polar form ( $Z\angle\theta$ ) (iii) the power factor (iv) the reactive power and (v) the apparent power. CO2 (08)
- c) Draw the impedance triangle of RL series circuit and hence deduce the expression for active, reactive and apparent powers. CO2 (04)

## UNIT- IV

7. a) Explain the working principle of a transformer. CO3 (06)
- b) Define slip of an induction motor. A three phase induction motor has 2 poles and is connected to a  $50Hz$ ,  $400V$  system. Calculate the actual rotor speed and rotor frequency when the slip is  $4\%$ . CO3 (08)
- c) Explain the construction of squirrel cage rotor with necessary diagram. CO3 (06)
8. a) Explain the concept of rotating magnetic field with relevant phasor diagram. CO3 (08)
- b) List out any three advantages of 3 phase AC. CO1 (06)
- c) A single phase  $25kVA$ ,  $2000/200V$  has iron and copper losses of  $350W$  and  $400W$  respectively. Calculate the efficiency at  $0.8$  power factor lagging. CO3 (06)

## UNIT - V

9. a) What is miniature circuit breaker? List any two merits and demerits of it. CO5 (06)
- b) What is two-way switch? Explain the working of it with neat sketch. CO4 (08)
- c) Define two-part tariff. Discuss how two-part tariff imposed to calculate electricity bills of domestic consumers. CO4 (06)
10. a) List any six safety precautions while working with electricity. CO5 (06)
- b) What is earthing? Explain the necessity of it. CO5 (08)
- c) Discuss the difference between earthing and grounding. CO5 (06)

\*\*\*\*\*